

VHDL: A “Crash” Course

Dr. Manuel Jiménez

With contributions by: Irvin Ortiz Flores




Electrical and Computer Engineering Department
University of Puerto Rico - Mayaguez



Outline

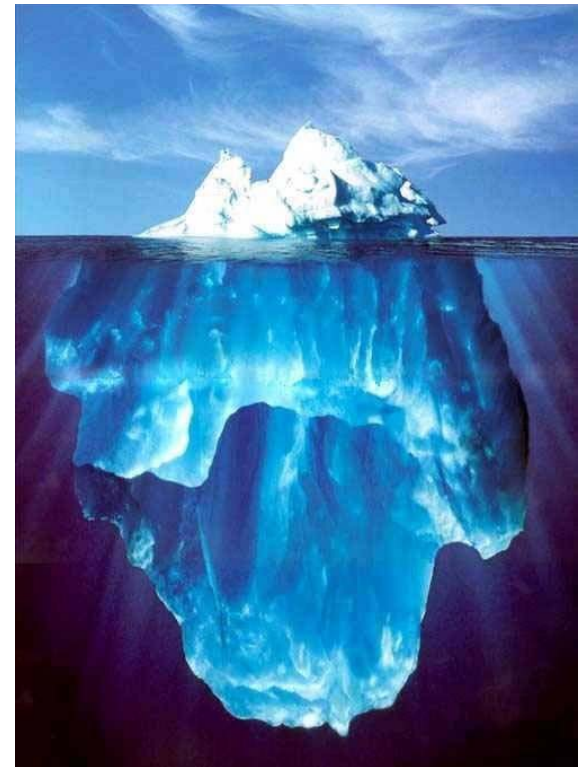- Background
- Program Structure
 - Types, Signals and Variables
- Description Styles
- Combinational Logic Design
- Finite State Machines
- Testbenches



What is VHDL?




- **VHDL:** VHSIC Hardware Description Language
 - VHSIC= Very High Speed Integrated Circuit
- VHDL was created for modeling digital systems
 - Language subset used in HW synthesis
- Hierarchical system modeling
 - Top-down and bottom-up design methodologies

VHDL Retrospective


- VHDL is an IEEE and ANSI standard for describing digital systems
- Created in 1981 for the DoD VHSIC program
 - First version developed by IBM, TI, and Intermetric
 - First release in 1985
 - Standardized in 1987 and revised several times thereafter
 - Standard 1076, 1076.1 (VHDL-AMS), 1076.2, 1076.3
 - Standard 1164, VHDL-2006
 - Inherits many characteristics of ADA: Strong typed

VHDL Uses

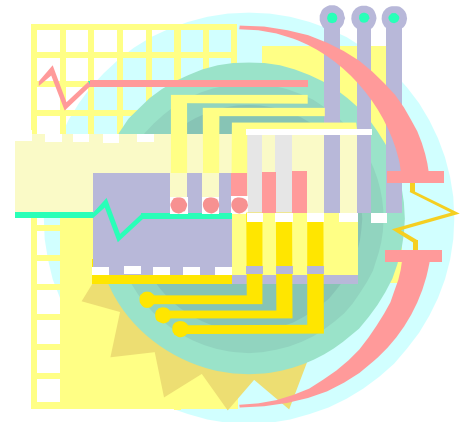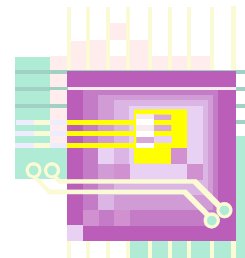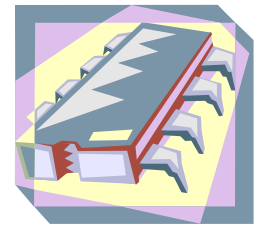- Modeling of Digital Systems
 - Looks a High-level Language
- Synthesis of Digital Systems
 - Language Subset
- Synthesis Targets
 - FPGAs & FPLDs
 - ASICs
 - Custom ICs



VHDL-based Design Flow

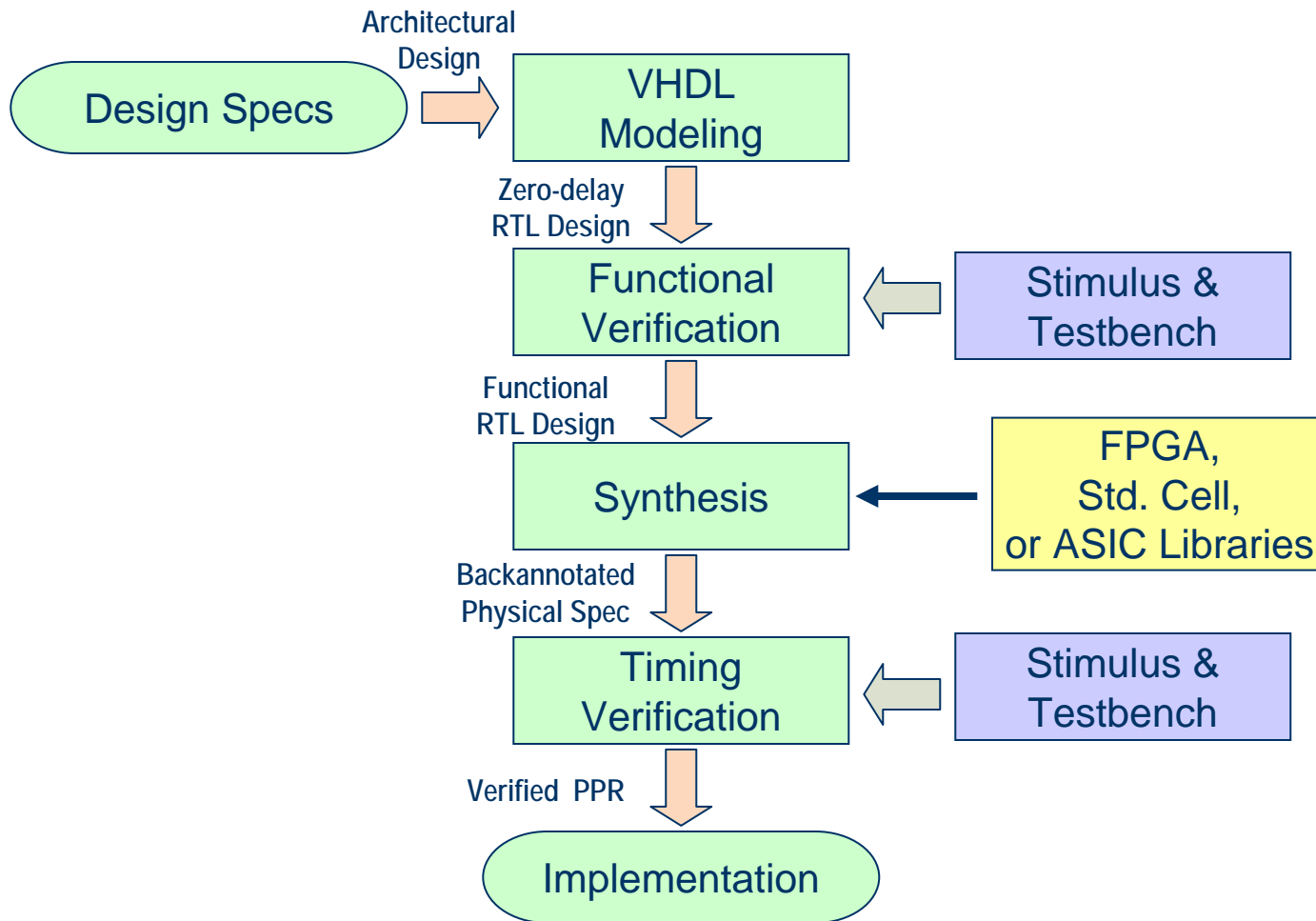

Common VHDL Data Types

- Integer: Predefined in the range $-(2^{31})$ through $+(2^{31}-1)$. Subtypes can be declared
- Boolean: False, True
- Bit, std_logic: A single bit
- Bit_vector, std_logic_vector: Multiple bits
 - Range needs to be specified

Basic VHDL Program Structure

Library Inclusion

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.STD_LOGIC_ARITH.all;
```

Entity Declaration

```
Entity Adder is  
    port (A,B : in std_logic_vector(4 downto 0);  
          Cin : in std_logic;  
          Sum : out std_logic_vector(4 downto 0);  
          Cout : out std_logic);  
End Adder;
```

Architecture Declaration

```
architecture a_adder of adder is  
    signal AC,BC,SC : std_logic_vector(5 downto 0);  
begin  
    AC <= '0' & A;  
    BC <= '0' & B;  
    SC <= unsigned(AC) + unsigned(BC) + Cin;  
    Cout <= SC(5);  
    Sout <= SC(4 downto 0);  
end a_adder;
```


Entity Declaration

- Specifies interface
- States port's name, mode, & type
- Mode can be IN, OUT, or INOUT
- Port type can be from a single bit to a bit vector

```
ENTITY Adder IS
  PORT (A,B : IN  STD_LOGIC(4 DOWNT0 0);
        Cin : IN  STD_LOGIC;
        Sum : OUT STD_LOGIC(4 DOWNT0 0);
        Cout : OUT STD_LOGIC);
END Adder;
```


Entity name

Port length

Port names

Port mode

Port type

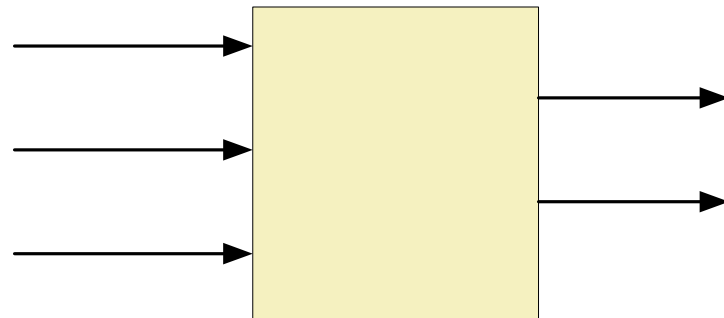

Architecture Declaration

- Describes the internal operation of an entity
- Several architectures can be associated to one entity
- States which components, signals, variables, and constants will be used

An Architecture Example

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.STD_LOGIC_ARITH.all;
```

→ Library declaration section

```
Entity Adder is
```

```
    port (A,B : in  std_logic_vector(4 downto 0);  
          Cin : in  std_logic;  
          Sum : out std_logic_vector(4 downto 0);  
          Cout : out std_logic);
```

```
End Adder;
```

→ Architecture declaration

```
architecture a_adder of adder is
```

→ Associated entity

```
    signal AC,BC,SC : std_logic_vector(5 downto 0);
```

→ Signal declaration. Also can be placed component, constants, types, declarations.

```
begin
```

```
    AC <= '0' & A;  
    BC <= '0' & B;  
    SC <= unsigned(AC) + unsigned(BC) + Cin;  
    Cout <= SC(5);  
    Sout <= SC(4 downto 0);
```

```
end a_adder;
```

→ Concurrent Statements:
Processed at the same time.
Also component instantiations,
and processes can be placed.

Signals Vs Variables (1/2)

- Signals

- Can exist anywhere, like wires
- Connect components or carry information between processes
- When inside a process, its value is updated when the process suspends
- Signal assignment operator: **<=**

- Variables

- Can only exist inside a process
- Behave like local HLL variables holding temporary values
- Values updated right after assignment. Sequence matters
- Variable assignment operator: **:=**

Concurrent Vs. Sequential Code

- Concurrent Statements
 - Occur typically outside a process
 - Take place concurrently, i.e. with simulation clock stopped
 - Uses of SIGNALS and processes
- Sequential Statements
 - Occur only inside a process
 - Are executed sequentially, i.e. one after another
 - Uses VARIABLES and functions

Signals Vs Variables (2/2)

- Signals

- Initial values: A=5, B=15, X=10
- Final values: A=10, B=5

```
Sigproc: process(A,X)
Begin
    A <= X;
    B <= A;
End process Sigproc;
```

- Variables

- Initial values: A=5, B= 15, X=10
- Final values: A=10, B=10

```
Sigproc: process(X)
Variable A,B : integer;
Begin
    A := X;
    B := A;
End process Sigproc;
```

Three-Bit Binary Counter

```
entity count1 is
    port( clock, enable: in bit;
          qa: out integer range 0 to 7);
end count1;
```

```
architecture countarch of count1 is
begin
```

```
    process (clock)
```

```
        variable count: integer range 0 to 7;
```

```
        begin
```

```
            if (clock'event and clock = '1') then
```

```
                if enable = '1' then
```

```
                    count := count + 1;
```

```
                end if;
```

```
            end if;
```

```
            qa <= count after 10 ns;
```

```
        end process;
```

```
    end countarch;
```


Sensitivity list. Process is executed each time one of this parameters change.

Variable declaration

Variable assignment operator

Sequential statements.

Signal assignment operator

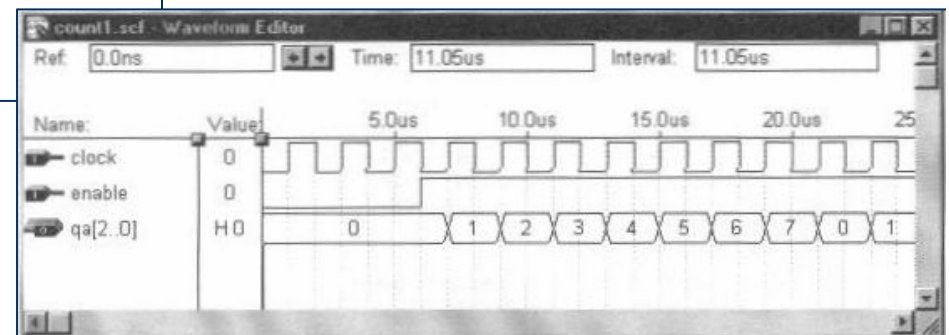


A “D” Flip-Flop

```
entity dff is
port ( d,clock : in bit;
      q: out bit);
end dff;

architecture arch of dff is
begin
  process (clock)
  begin
    if(clock'event and clock=1) then
      if(d='1') then
        q <= '1';
      else
        q <= '0';
      end if;
    end if;
  end process;
end arch;
```

Refers to the rising edge of the clock

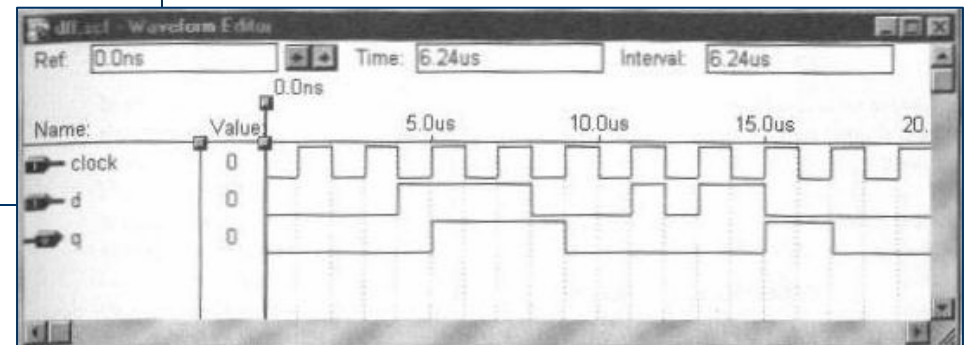Explicit comparisons and assignments to port and signals uses ' ' for one bit and “ ” for multiple bits




D-type flip-flop with active low preset and clear inputs

```
-- The pm and din signals are asynchronous
entity dffpc is
    port(d,clrn,prn,clk: in bit;
          q out bit);
end dffpc;
architecture arch of dffpc is
begin
    process (clk)
    begin
        if(clk'event and clk = '1') then
            if(d='1' and prn='1' and clrn='1') then
                q <= '1';
            elsif(d='0' and prn='1' and clrn='1') then
                q <= '0';
            end if;
            --handle active low preset
            if(prn='0' and clrn='1') then
                q <= '1';
            end if;
            --handle active low clear
            if(clrn='0' and prn='1') then
                q <= '0';
            end if;
        end if;
    end process;
end arch;
```

Comments begin with --

Logical operators *and*, *or*, *not*, *nand*, *xor* are defined in the language

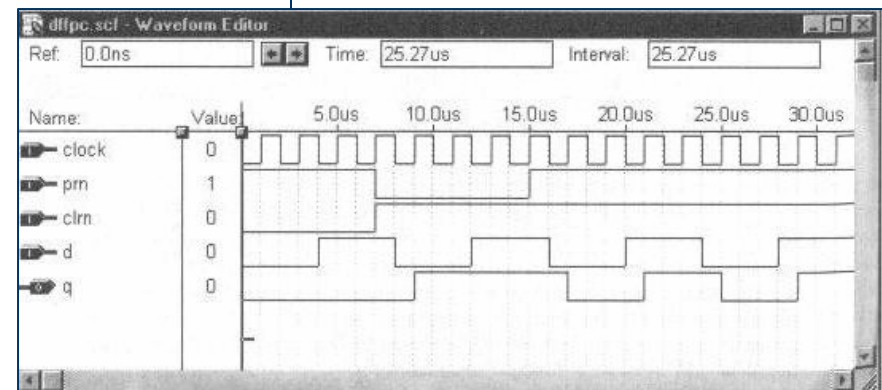
elsif is used instead of the *else if* of C language.



D Flip-Flop with Asynchronous Preset and Clear

```
entity dffapc is
    port(clock, d, prn, clrn : in bit;
          q : out bit);
end dffapc;
architecture arch1 of dffapc is
begin
    process(clock, clrn, prn)
        variable reset, set: integer range 0 to 1;
    begin
        if(prn='0') then
            q <= '1';
        elsif (clrn='0') then
            q <= '0';
        elsif (clock'event and clock='1') then
            q <= d;
        end if;
    end process;
end arch1;
```

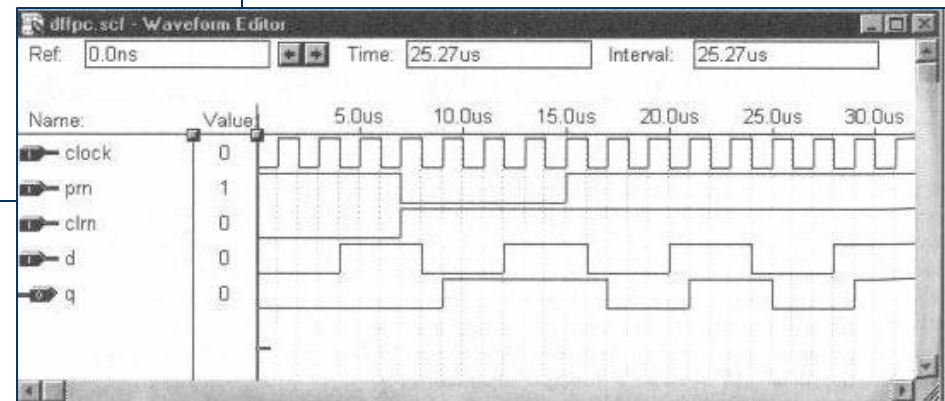
Integer range definition. Range 0 to 1 defines one bit.



Full Adder

```
library ieee;
use ieee.std_logic_1164.all;
entity fulladd is
    port( a1,a2,cin: in std_logic;
          sum,cout: out std_logic);
end fulladd;

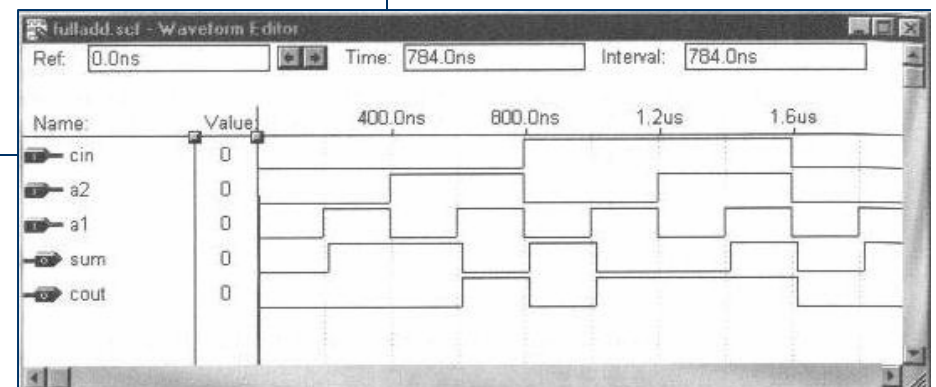architecture fulladd of fulladd is
begin
    process(a1,a2,cin)
    begin
        sum <= cin xor a1 xor a2;
        cout <= (a1 and a2) or (cin and (a1 xor a2));
    end process;
end fulladd;
```




Four Bit Adder

```
--A VHDL 4 bit adder
entity fourbadd is
    port ( cin: in integer range 0 to 1;
          addend1:in integer range 0 to 15;
          addend2:in integer range 0 to 15;
          sum: out integer range 0 to 31);
end fourbadd;
architecture a4bitadd of fourbadd is
begin
    sum <= addend1 + addend2 + cin;
end a4bitadd;
```

Integer type allows addition, subtraction and multiplication. Need the following statement at the library declaration section:

use IEEE.STD_LOGIC_ARITH.all

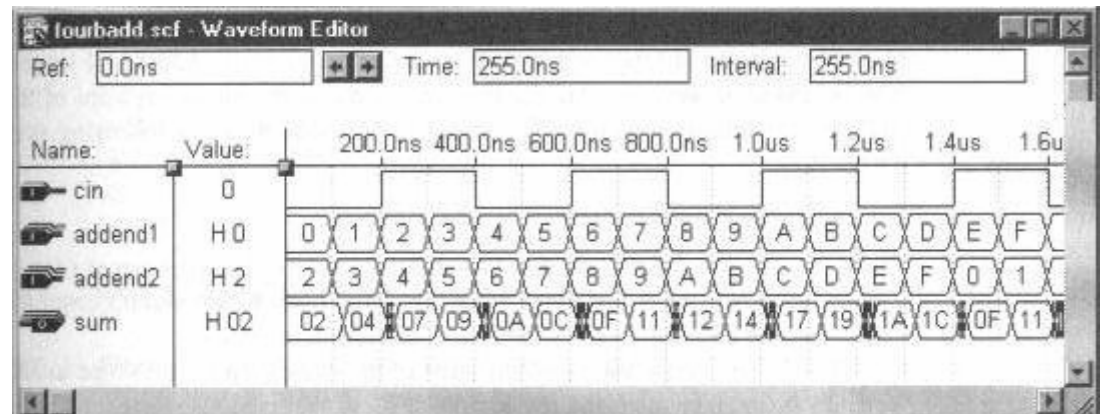


VHDL Description Styles

- Dataflow: Uses concurrent signal assignments
- Behavioral: Relies on process to implement sequential statements
- Structural: Describes the interconnections among components of a system. Requires hierarchical constructs.
- Mixed Method: Combines the three styles.

D Flip-Flop Dataflow

```
--D flip-flop dataflow
--Includes preset and clear
entity dff_flow is
    port ( d, prn, clrn: in bit;
          q,qbar: out bit);
end dff_flow;

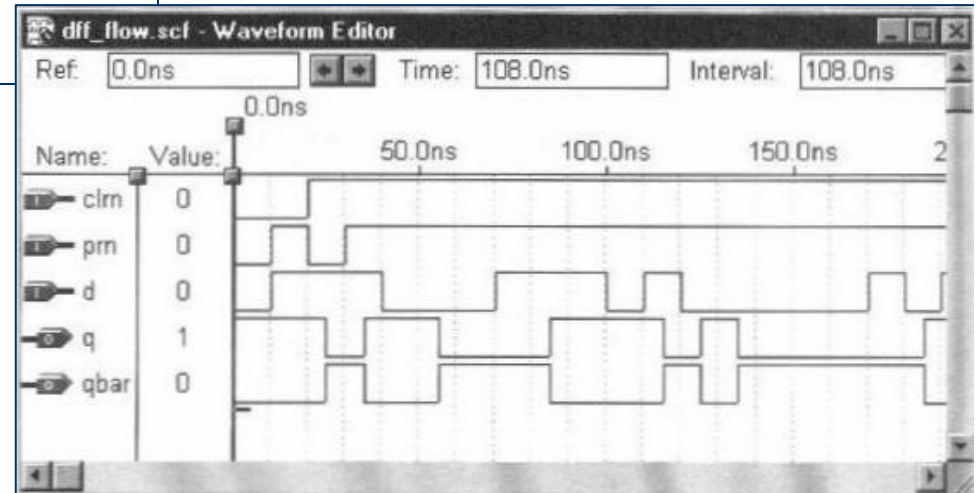
architecture arch1 of dff_flow is
begin
    q <= not prn or (clrn and d);
    qbar <= prn and (not clrn or not d);
end arch1;
```



Behavioral D Flip-Flop

```
--Active low preset and clear inputs
entity dffpc2 is
    port(d,clock,clrn,prn:in bit;
        q,qbar:out bit;
end dffpc2;

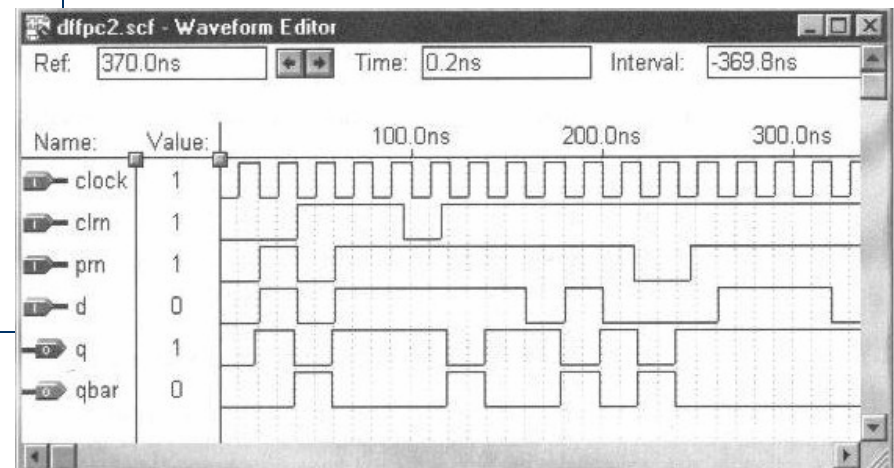architecture arch of dffpc2 is
begin
    process(clock,clrn,prn)
        begin
            if(clock'event and clock = '1')
            then
                q <= not prn or (clrn and d);
                qbar <= prn and (not clrn or
                    not d);
            end if;
        end process;
    end arch;
```



D Flip-Flop Structural

```
entity dff_str is
    port (d :in bit;
          q,qbar:out bit);
end dff_str;

architecture adff_str of dff_str is
    component nandtwo
        port(x, y: in bit;
             z:out bit);
    end component;

    signal qbarinside, qinside, dbar: bit;
begin
    nandq:nandtwo
    port map(qinside, d,qbarinside);

    nandqbar:nandtwo
    port map(qbarinside,dbar, qinside);


    dbar <= not d;
    q <= qinside;
    qbar <= qbarinside;
end adff_str;
```

Component declaration. Port appears exactly as in the entity declaration.


Entity name

Component instantiation label

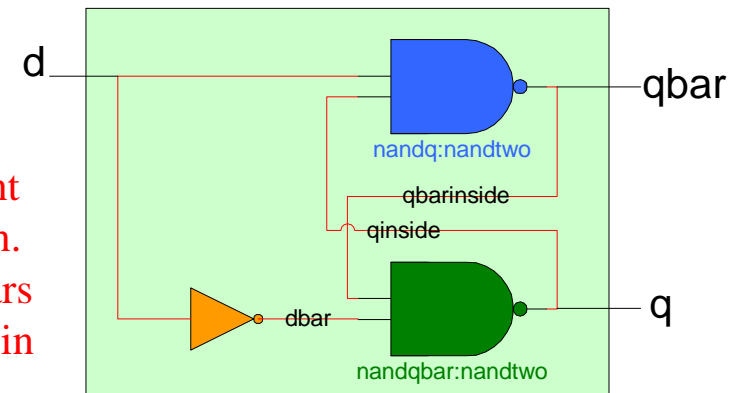Component instantiation. Connections are made by correspondence


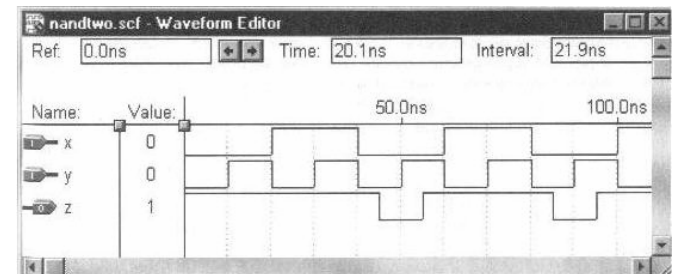
```
--A two input nand gate
entity nandtwo is
    port(x, y:in bit;
          z :out bit);
end nandtwo;
architecture anandtwo of nandtwo
is
begin
    z <= not(x and y);
end anandtwo;
```



A Sequence Detector

```

entity simple is
port (    clock, resetn, w: in stdlogic;
        z:out std logic);
end simple;

architecture behavior of simple is
type state_type is (a, b, c);
signal y: state_type ;
begin
    process (resetn, clock)
    begin
        if resetn = '0' then
            y <= a;
        elsif (clock'event and clock = '1') then
            case y is
            when a =>
                if w='0' then
                    y <= a;
                else
                    y <= b;
                end if;
            end case;
        end if;
    end process;
end behavior;


```

Type declaration

Signal definition using a defined type

Case statement declaration

Item under test

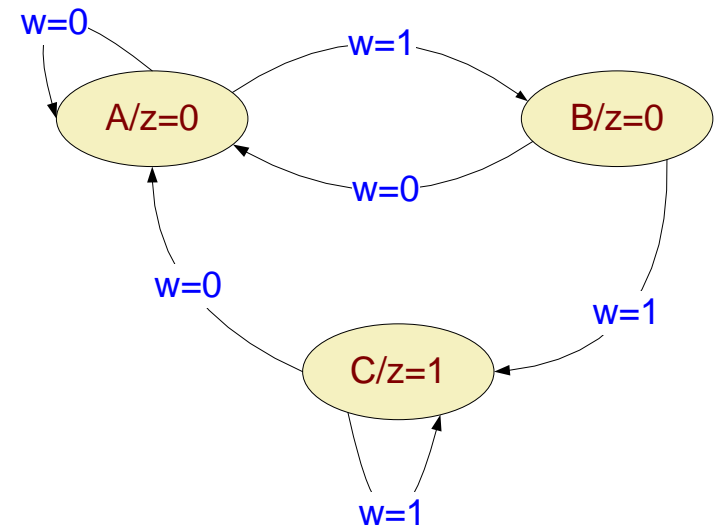


Clock Cycle	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
W:	0	1	0	1	1	0	1	1	1	0	1
Z:	0	0	0	0	0	1	0	0	1	1	0

A Sequence Detector (continued)

```
when b =>  
  if w='0' then  
    y <= a;  
  else  
    y <= c;  
  end if;  
when c =>  
  if w='0' then  
    y <= a;  
  else  
    y <= c;  
  end if;  
end case;  
end if;  
end process;  
z <= '1' when y=c else '0';  
end behavior;
```

Case statement declaration

Conditional signal assignment

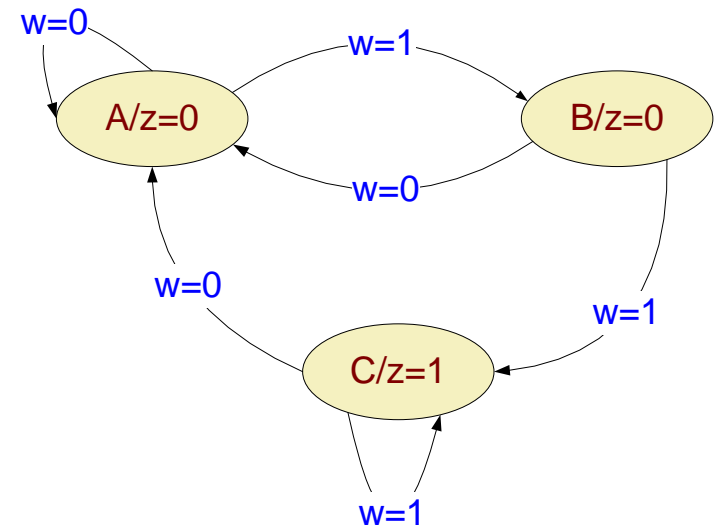


Clock Cycle	t ₀	t ₁	t ₂	t ₃	t ₄	t ₅	t ₆	t ₇	t ₈	t ₉	t ₁₀
W:	0	1	0	1	1	0	1	1	1	0	1
Z:	0	0	0	0	0	1	0	0	1	1	0

Testbenches

- Stimuli transmitter to DUT (testvectors)
- Needs not to be synthesizable
- No ports to the outside
- Environment for DUT
- Verification and validation of the design
- Several output methods
- Several input methods

Example of a testbench

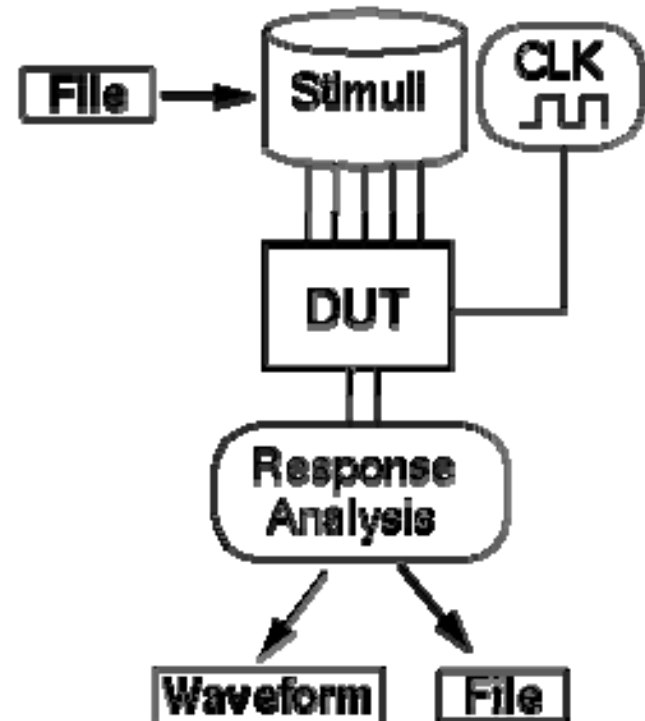

Example Testbench

```
entity TB_TEST is
  end TB_TEST;
architecture BEH of TB_TEST is
  -- component declaration of the DUT
  -- internal signal definition
begin
  -- component instantiation of the DUT
  -- clock generation
  -- stimuli generation
end BEH;
```

Example Testbench

```
entity TB_TEST is
end TB_TEST;

architecture BEH of TB_TEST is
  component TEST
    port(CLK      : in std_logic;
         RESET    : in std_logic;
         A        : in integer range 0 to 15;
         B        : in std_logic;
         C        : out integer range 0 to 15);
  end component;

  constant PERIOD : time := 10 ns;
  signal W_CLK     : std_logic := '0';
  signal W_A, W_C  : integer range 0 to 15;
  signal W_B       : std_logic;
  signal W_RESET   : std_logic;
begin
  DUT : TEST
    port map(CLK      => W_CLK,
             RESET    => W_RESET,
             A        => W_A,
             B        => W_B,
             C        => W_C);
  ...
end;
```



Questions?